CICS 290M (F19) Homework 7

For any question involving calculation, you <u>MUST</u> write down at least one line of derivation (i.e. how you derived the answer). If you write down a number without any derivation, you will receive 0. [2+2+2+3+3+8=20pts]

1. What is a <u>reed sensor</u> for? Name <u>two applications</u> of reed sensor. [2pts]

Reed sensor is built using a reed switch for additional functionality.

2. What is an H-bridge used for? How many transistors do you need to make an H-bridge? [2pts]

H-Bridge is used to change the polarity of voltage applied to a load. You need for transistors to make an H-bridge.

3. What is a servo motor? What component does the servo use to tell its current angular position? [2pts]

It is a motor with a built-in encoder and feedback circuit for working with angular positions. The encoder(potentiometer) provides the current angular position.

4. [This problem has nothing to do with electronics, nonetheless, it's a classic problem to practice equation solving skills]. Some chickens and rabbits got mixed into a cage. An advanced computer sensor detected that there are 35 heads and 94 legs. How many chicken and rabbits are there respectively? [Hint: obviously a chicken has 2 legs and a rabbit has 4 legs]. [3pts]

```
Let x be chickens and y be rabbits

x+y = 35

2x+4y = 94

=> x + 2y = 47

=> y = 12 and x = 35-12 = 23
```

5. We have two resistors of unknown values, but we do know that their **series resistance** (i.e. total resistance when they are connected in series) **is 20 ohm** and the **parallel resistance is 3.2 ohm**. What are the two resistor values respectively? [3pts]

```
a+b = 20 = series resistance, where a and b are the resistors 1/a + 1/b = 1/(3.2) => a+b/ab = 1/(3.2) =>ab/20 = 3.2 => ab = 64. (a+b)<sup>2</sup> = 20^2 = 400 (a+b)<sup>2</sup> -4ab = (a-b)<sup>2</sup> =>400 - 4*64 = (a-b)<sup>2</sup> = 144 -> a-b = 12 a + b = 20, a - b = 12 2a = 32, a = 160hms, b = 40hms
```

[Continue to the next page]


CICS 290M (F19) Homework 7

- **6.** A typical thermistor (TDR) has a nominal value of $100K\Omega$. Its <u>datasheet can be found here</u>. Using the datasheet, answer the following questions: [8pts]
- a) If at some room, the resistance of the TDR is $161K\Omega$. What's the <u>room temperature at this moment in Celsius</u> (°C)? [Hint: just use the closest number in the table, no need to interpolate, 1pt]

```
15.00
```

b) To use ESP32 to measure temperature with this TDR, we adopt a voltage divider circuit shown on the right. The **power supply voltage is 3.3V**, and the **fixed resistor R=100K\Omega**. Write down the expression for Vout in terms of TDR. [2pts]

```
V_{out} = V_{PS} * TDR/(TDR+R)
```

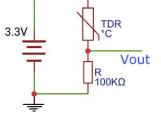

c) We use ESP32's analog pin to measure Vout. If the **analog reading is ADC**, <u>write down the expression for TDR in terms of ADC</u>. [Recall that the analog reading ADC is 0 when the measured voltage is 0.0V, and 4096 when measured voltage is 3.3V, and everything in between scales linearly]. [1pt]

```
ADC = V<sub>out</sub> * 4096/3.3

V<sub>out</sub> = V<sub>ps</sub> * TDR/(TDR+R)

= 3.3 *TDR/(TDR+100K)

=> ADC = 3.3*(4096/3.3)*TDR/(TDR+100K)

= 4096*TDR/(TDR+100K)
```

d) If we put the circuit in a room, and ESP measured **ADC=2048**, 1) what's the value of TDR at the moment? 2) using the datasheet again, find out the temperature in Celsius (°C). [2pts]

```
1) ADC = 4096*TDR/(TDR+100K) = 2048

=> TDR/(TDR+100K) = ½

=>(TDR+100K)/TDR = 2

=>1+100K/TDR = 2

=>100K/TDR = 1

=>TDR = 100K

2) 25 degrees C
```

e) We put the circuit in a freezer, and Arduino measured **ADC=585**, 1) what's the value of TDR at the moment? 2) using the datasheet again, find out the temperature in Celsius (°C). [2pts]

```
1) ADC = 4096*TDR/(TDR+100K) = 585

=> TDR/(TDR+100K) = 585/4096

=>(TDR+100K)/TDR = 4096/585

=>1+100K/TDR = 4096/585

=>100K/TDR = 4096/585-1

=> TDR = 100K/6.00170940171

=> TDR = 16.66K

2) 69.44 degrees C
```